

國立臺北科技大學

九十六學年度電資碩士在職專班招生考試

電子學 試題

填 准 考 證 號 碼

第一頁 共二頁

--	--	--	--	--	--	--

注意事項：

1. 本試題共【6】題，配分共 100 分。
2. 請按順序標明題號作答，不必抄題。
3. 全部答案均須答在答案卷之答案欄內，否則不予計分。

I. What is the correct answer? (25%)

- (1). If the width of an NMOS transistor increases, the current will
(a). increase (b). decrease (c) not change
- (2). If the supply voltage of a chip increases, the gate capacitance of each transistor will
(a). increase (b). decrease (c) not change
- (3). In active region of MOSFET, the drain current will be increased slightly, why?
(a). Channel charge (b). Early effect (c) Channel length modulation
- (4). If the temperature increases, the magnitude of the threshold voltage will
(a). increase (b). decrease (c) not change
- (5). If an NMOS is used to be a switch, the larger the input voltage is, the impedance will
(a). increase (b). decrease (c) not change

2. For the circuit in Fig. 2, find the voltage gain v_o/v_i , and the power gain P_L/P_I . (15%)

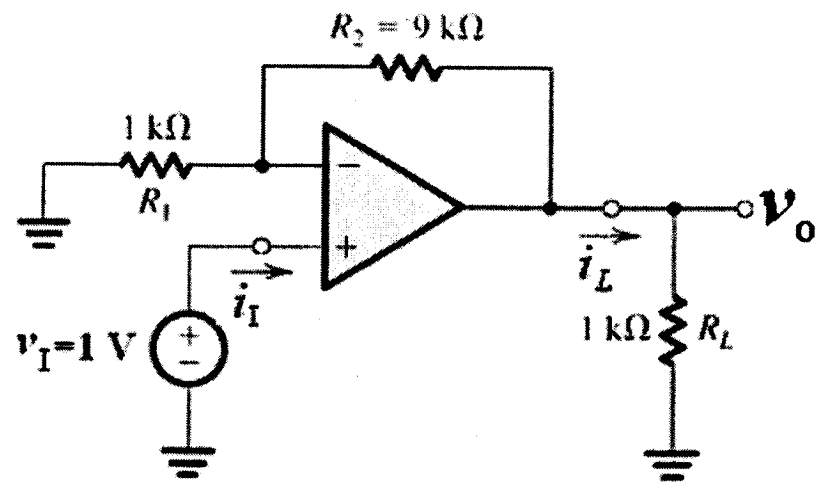


Figure 2

3. Assume that the coupling capacitors, C_{C1} , C_{C2} , and C_E , are sufficiently large. Find the input resistance R_{in} , the voltage gain A_v ($\alpha \approx 1$), the output resistance R_{out} , the overall voltage gain G_v , and the short-circuit current gain A_{is} , respectively. (15%)

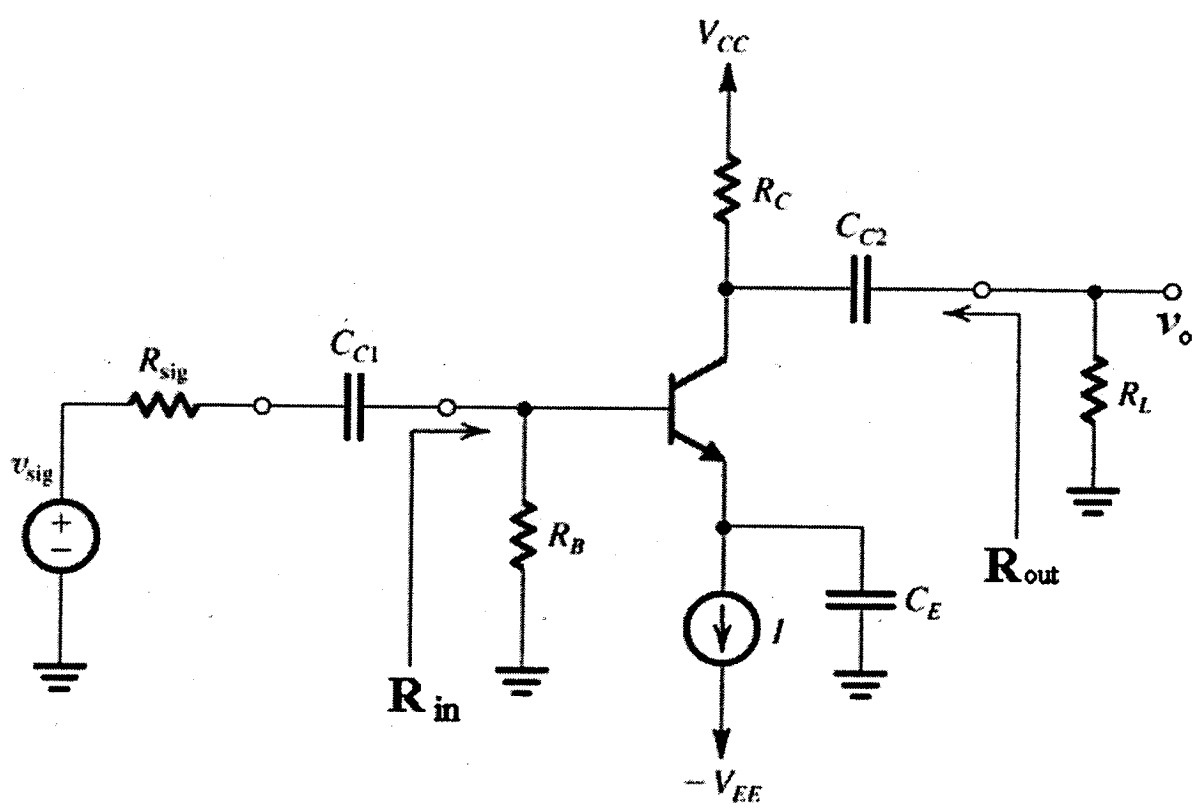


Figure 3

注意：背面尚有試題

4. A simplified small-signal equivalent circuit is shown in Fig. 4. Find the amplifier transfer function V_o/V_{id} , the zero s_z , the dominant pole ω_{p1} , the nondominant pole ω_{p2} , and the unity-gain frequency ω_t , respectively. (15%)

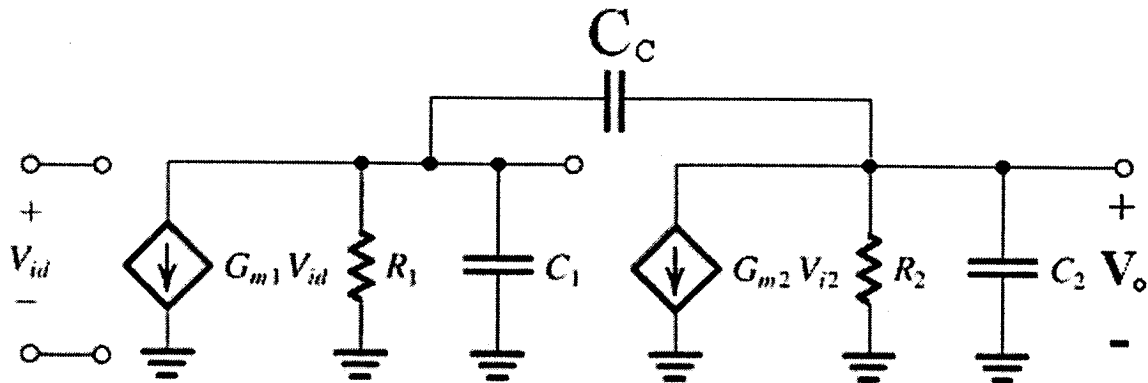


Figure 4

5. For the circuit of Fig. 5, let $V_{DD} = V_{SS} = 1.5$ V, $V_m = 0.6$ V, $V_{tp} = -0.6$ V, all channel lengths = $1 \mu\text{m}$. $K'_n = 200 \mu\text{A}/\text{V}^2$, $k'_p = 80 \mu\text{A}/\text{V}^2$, and $\lambda = 0$. For $I_{REF} = 10 \mu\text{A}$, find the widths of all transistors to obtain $I_2 = 60 \mu\text{A}$, $I_3 = 20 \mu\text{A}$, and $I_5 = 80 \mu\text{A}$. It is further required the voltage at the drain of Q_2 be allowed to go down to within 0.2 V of the negative supply and that the voltage at the drain of Q_5 be allowed to go up to within 0.2 V of the positive supply. (15%)

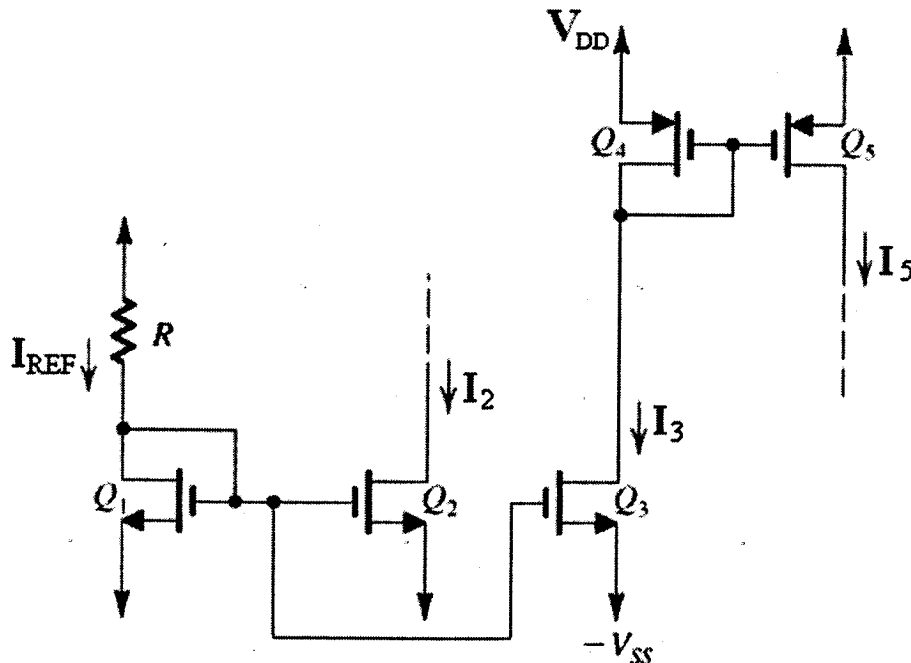


Figure 5

6. The shunt-shunt feedback amplifier in Fig. 6 has $I = 1 \text{ mA}$ and $V_{GS} = 0.8 \text{ V}$. The MOSFET has $V_t = 0.6 \text{ V}$ and $V_A = 30 \text{ V}$. For $R_S = 10 \text{ k}\Omega$, $R_1 = 1 \text{ M}\Omega$, and $R_2 = 4.7 \text{ M}\Omega$, find the voltage gain v_o/v_s , the input resistance R_{in} , and the output resistance R_{out} . (15%)

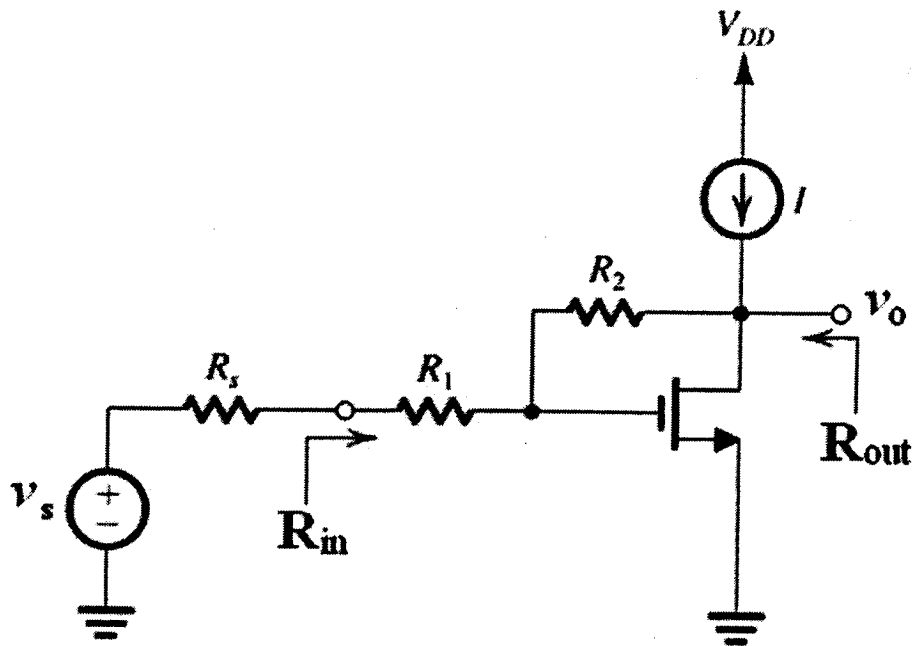


Figure 6